

Section 2.4: Logic Circuits and

Friday, January 17, 2020 10:56 AM

Boolean Algebra

logic circuit: an electrical circuit with only two levels

- one voltage is set at zero volts (grounded)
- the other is set to some other value, such as five volts

two values: 5 volts / zero volts
 on / off
 1 / 0

a little bit of background (will not be tested):

the circuit behaves like a switch:




Consider the two circuits below:



behaves like "and" - need

"and" - need both closed

 


behaves like "or".
need at least one closed

gate representation

(this I will test)


"and"

 

← the dot means "and"

← also okay to write just AB with no dot

"or"

 


← "plus" means "or"


"not"




← the overline (or bar) " "

 

 
example: give the output for the following circuits




$$\overline{A + B}$$

 

$$A\overline{B}$$

 
 
$$\overline{\overline{A} + \overline{B}}$$




$$\overline{\overline{A} \overline{B} C}$$

2020/01/21

draw the gate representation for $A + \overline{B} \overline{C}$

 note: do "and"
before "or",
just as before



Boolean Algebra

- algebra in which the variables can only take on one of two possible values: 0 and 1

"and" symbol is a dot •

or implied multiplication (no symbol)

$$A \cdot B, AB, A \cdot 0$$

"or" symbol is + (plus sign)

$$A + B$$

"not" symbol is —

$$\bar{A} \quad \overline{AB}$$

order of operations

"and" before "or" (just like before)

the negation bar behaves like brackets

you can use brackets to force the order that you want

example : which operation comes first?

①

$$A + BC$$

"and" first, then "or"

②

$$(A + B)C$$

"or" first, then "and"

③

$$\overline{A + B} C$$

↑
"or", then "not", then "and"

④

$$A + \overline{B} C$$

↑
"not", then "and", then "or"

⑤

$$\overline{AB}$$

↑
"and", then "not"

example: write the truth table for $A + \overline{B} \overline{C}$

A	B	C	\overline{B}	\overline{C}	$\overline{B} \overline{C}$	$A + \overline{B} \overline{C}$
0	0	0	1	1	1	1
0	0	1	1	0	0	0
0	1	0	0	1	0	0
0	1	1	0	0	0	0
1	0	0	1	1	1	1
1	0	1	1	0	0	1
1	1	0	0	1	0	1
1	1	1	0	0	0	1