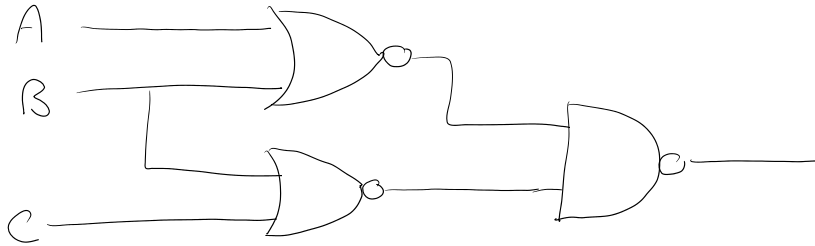


Chapter 2 Review Questions

Thursday, October 05, 2023 4:32 PM

Consider the following logic circuit



a) Write the Boolean expression that is the output of this circuit

$$\overline{\overline{A+B} \overline{B+C}}$$

b) Simplify this expression using the laws of log.c.

method #1

$$\overline{\overline{A+B} \overline{B+C}}$$

$$\overline{\overline{A} \overline{B} \overline{B} \overline{C}} \quad \text{DeMorgan's}$$

$$\overline{\overline{A} \overline{B} \overline{C}} \quad \text{idempotent}$$

$$\overline{(\overline{A} \overline{B}) \overline{C}} \quad \text{associative}$$

$$\overline{\overline{A} \overline{B}} + C \quad \text{DeMorgan's}$$

$$A+B+C \quad "$$

method #2

$$\overline{\overline{A+B} \overline{B+C}}$$


$$A+B + B+C \quad \text{DeMorgan's}$$

$$A+B+C \quad \text{idempotent}$$



c) Draw a logic circuit that has this simplified

c) Draw a logic circuit that has this simplified expression as a result.

$$A + B + C$$

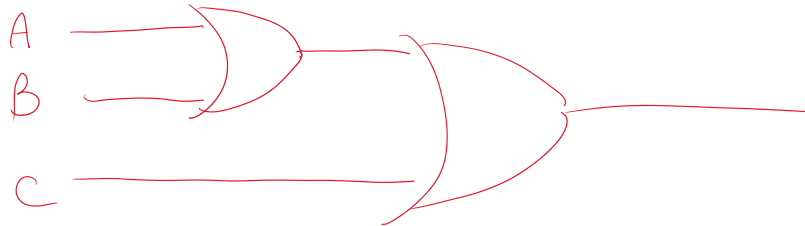

or

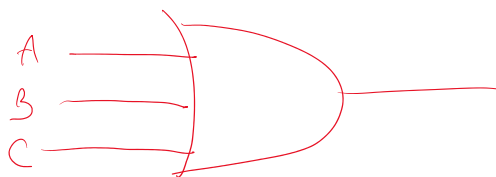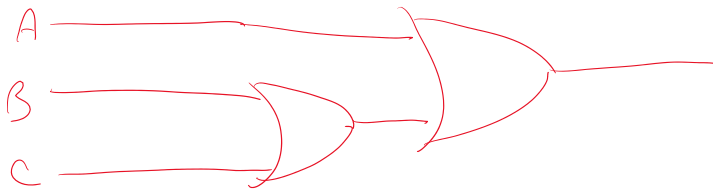

Simplify using the L.O.L.

$$AC(\bar{A} + B + \bar{C}) + A\bar{B}C$$

$$AC\bar{A} + ACB + AC\bar{C} + A\bar{B}C$$

distributive

$$C \cdot 0 + ACB + A \cdot 0 + A\bar{B}C$$

complement

$$0 + ACB + 0 + A\bar{B}C$$

identity

$$ACB + A\bar{B}C$$

h

$$ACB + A\bar{B}C$$

$$AC(B + \bar{B})$$

$$AC \cdot 1$$

$$AC$$

distrib

complement

identity