


Section 1.8: Gates

Friday, October 09, 2015
9:31 AM

example: draw the gate representation for

$$A + \overline{B} \overline{C}$$

note: do "and" before "or"

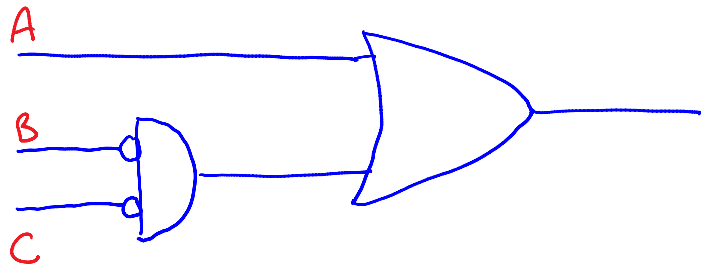

Boolean Algebra:

algebra in which the variables can only take one of two possible values: 0 or 1

"and": symbol is a dot \cdot or implied (no symbol)
example: $A \cdot B$ or just AB
 $A \cdot 1$

"or": symbol is a plus sign
example: $A + B$

"not": symbol is a bar above the variable or expression

order of operations:

"and" before "or" (like multiplication before addition)

the negation bar behaves like brackets

you can use brackets to force the order that you want

examples: state the order of operations:

① $A + BC$

↑
"and" then "or"

② $A + \overline{B}C$

↑
"not", then "and", then "or"

③ $\overline{A+B}C$

↑
"or" (A+B), then "not", then "and"

④ $\overline{AC} + B$

↑
"and", then "not", then "or"

example: write the truth table for $A + \overline{B}\overline{C}$

A	B	C	\overline{B}	\overline{C}	$\overline{B}\overline{C}$	$A + \overline{B}\overline{C}$
0	0	0	1	1	1	1
0	0	1	1	0	0	0
0	1	0	0	1	0	0
0	1	1	0	0	0	0
1	0	0	1	1	1	1
1	0	1	1	0	0	1
1	1	0	0	1	0	1
1	1	1	0	0	0	1