

Section 1.8: Logic Circuits and Boolean Algebra

Wednesday, October 01, 2014
3:14 PM

logic circuit: it's an electrical circuit with only two levels of voltage

- one level is set to zero volts

(grounded)

- the other is set to some non-zero value

(5V)

a little bit of background (will not be tested)

the circuit behaves like a switch:

